

FINAL PROJECT – INFORMATICA INDUSTRIALE

Group 2:

- Mattia Vincenzi
(860579)
- Francesco Porto
(816042)



OUTLINE

- Introduction
- Symbol
 - I/O ports
- Top-view block scheme
 - Internal signals
 - VHDL Design of all stages
- Simulation results
- Conclusion



OUTLINE

- **Introduction**
- Symbol
 - I/O ports
- Top-view block scheme
 - Internal signals
 - VHDL Design of all stages
- Simulation results
- Conclusion



INTRODUCTION


- Initial assumptions:
 - Red will be modulated along with Green
 - (i.e. setting MOD12 makes **both** Red and Green last 12 seconds)
 - We decided to add an initial **OFF state**
 - It can only be left by setting the MAINTENANCE state
 - A **FAULT** signal has been added to report errors (due to setting conflicting inputs)
 - We decided to set the clock period to 1 sec (1 Hz)
 - However, for testing purposes, we set it to 20 ns
 - Simulating a 1 sec clock period with ModelSim was too expensive



OUTLINE

- Introduction
- **Symbol**
 - I/O ports
- Top-view block scheme
 - Internal signals
 - VHDL Design of all stages
- Simulation results
- Conclusion

SYMBOL

 



OUTLINE

- Introduction
- **Symbol**
 - **I/O ports**
- Top-view block scheme
 - Internal signals
 - VHDL Design of all stages
- Simulation results
- Conclusion

I/O PORTS

Name	Direction	Resolution	Comment
Enable	Input	1	Active High, Synchronous.
Reset	Input	1	Active Low, Asynchronous.
Condition	Input	2	00 -> Maintenance 01 -> Nominal 11 -> Standby 10 not used
Modality	Input	2	00 -> MOD5 01 -> MOD12 11 -> MOD15 10 not used
Clk	Input	1	

I/O PORTS

Name	Direction	Resolution	Comment
Red	Output	1	
Yellow	Output	1	
Green	Output	1	
Fault	Output	4	0000 -> Enable is set to 0 0001 -> Everything working correctly 0010 -> Condition error 0100 -> Modality error 1000 -> Condition AND Modality error




OUTLINE

- Introduction
- Symbol
 - I/O ports
- **Top-view block scheme**
 - Internal signals
 - VHDL Design of all stages
- Simulation results
- Conclusion

TOP-VIEW BLOCK SCHEME

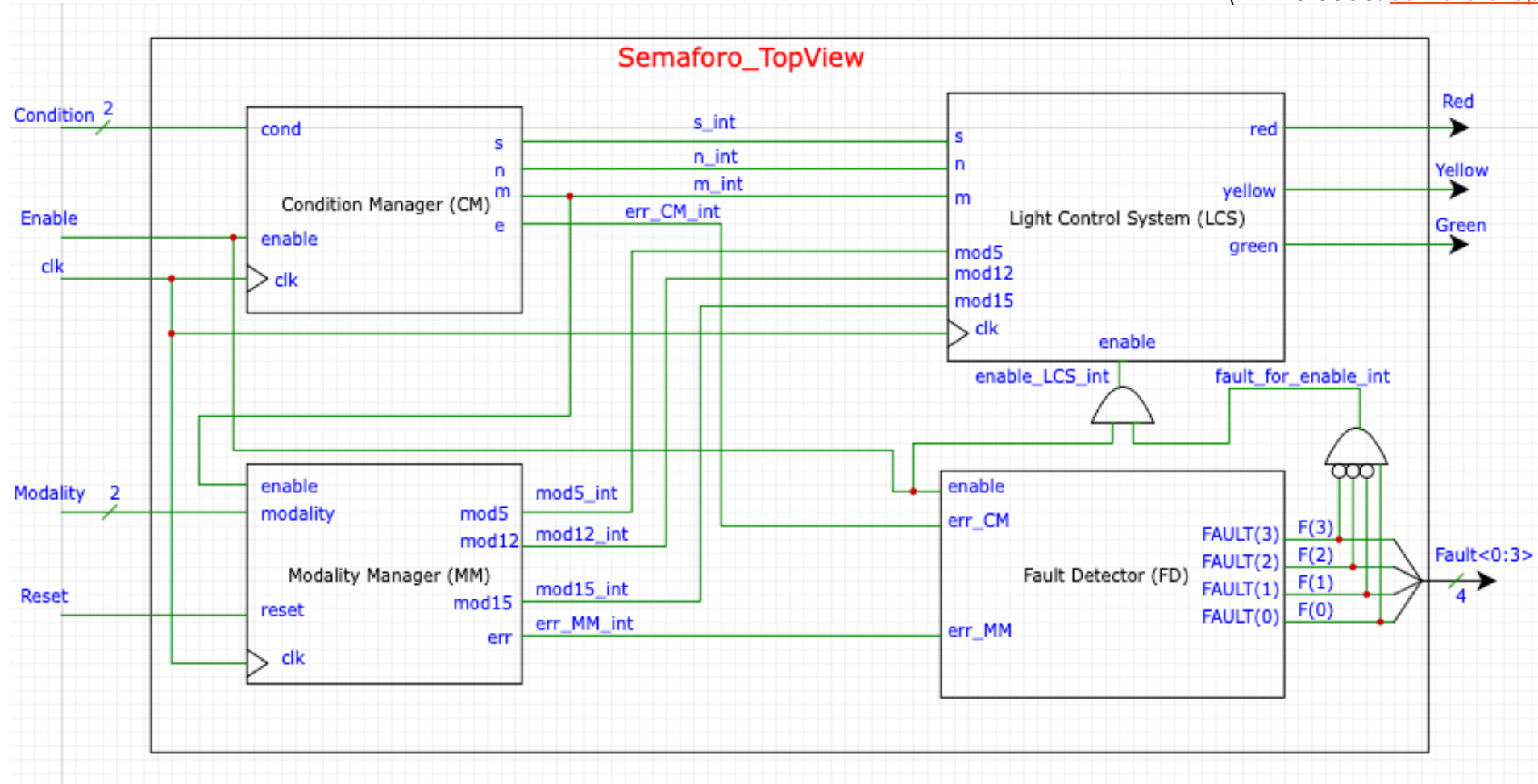(Link to code: [SemaforoTopView.vhdl](#))





OUTLINE

- Introduction
- Symbol
 - I/O ports
- Top-view block scheme
 - **Internal signals**
 - VHDL Design of all stages
- Simulation results
- Conclusion

INTERNAL SIGNALS

Name	Resolution	Comment
mod5_int	1	Connects MM and LCS. It is 1 when mod5 is set.
mod12_int	1	Connects MM and LCS. It is 1 when mod12 is set.
mod15_int	1	Connects MM and LCS. It is 1 when mod15 is set.
err_MM_int	1	Connects MM and FD. It is 1 when the input modality is 10.
m_int	1	Connects CM and LCS. It is 1 when MAINTENANCE is set.
n_int	1	Connects CM and LCS. It is 1 when NOMINAL is set.
s_int	1	Connects CM and LCS. It is 1 when STANDBY is set.
err_CM_int	1	Connects CM and FD. It is 1 when the input condition is 10.
fault_for_enable_int	1	It is 1 when FAULT is 0001 (everything works correctly)
enable_LCS_int	1	Enables LCS. It is 1 iff fault_for_enable_int AND (global) Enable.




OUTLINE

- Introduction
- Symbol
 - I/O ports
- Top-view block scheme
 - Internal signals
 - **VHDL Design of all stages**
- Simulation results
- Conclusion

CONDITION MANAGER

(Link to code: [ConditionManager.vhdl](#))

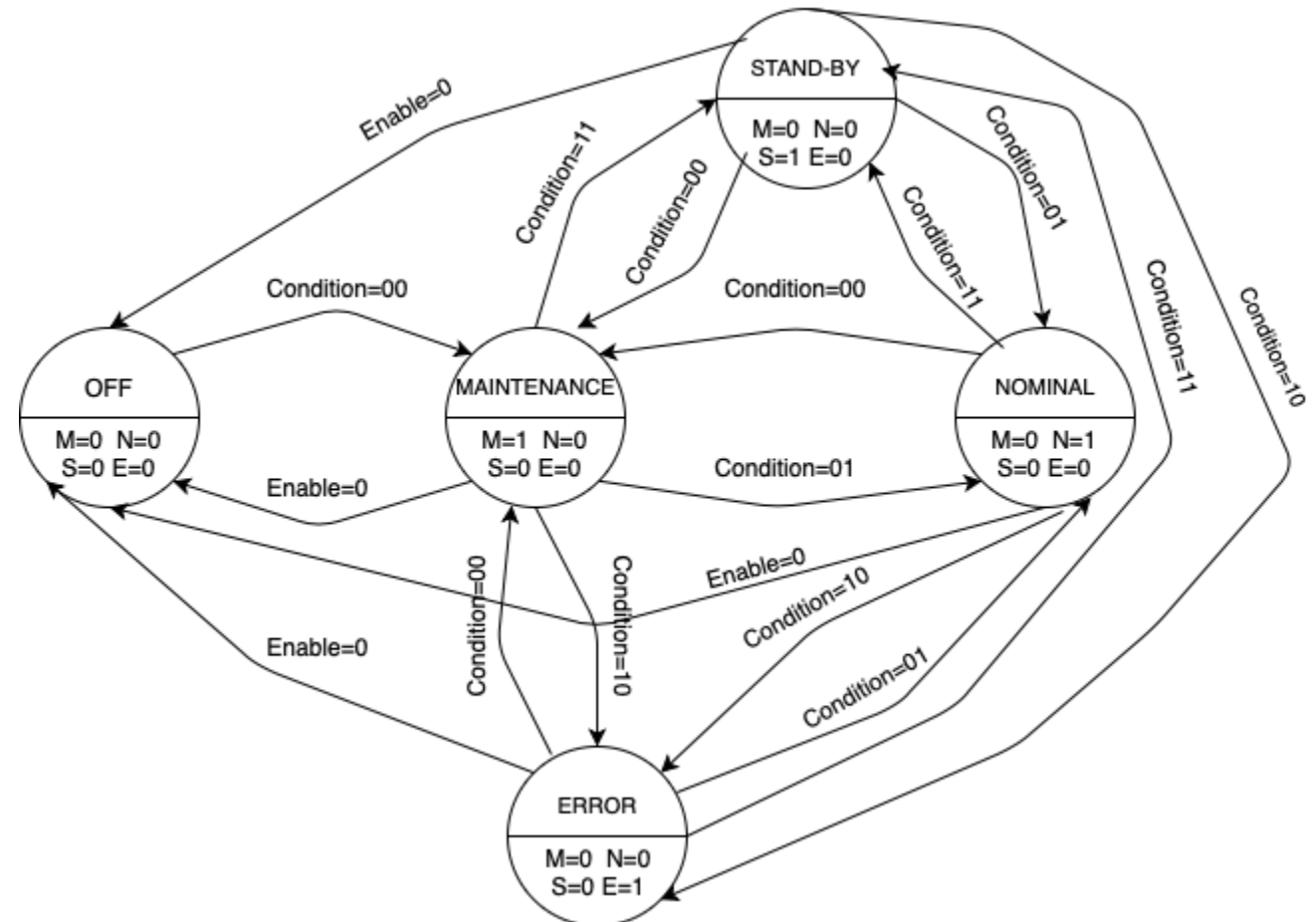- It is a **Moore FSM**
- The starting state is **OFF**, which can be left only by setting Condition to 00, thus entering the **MAINTENANCE** state
- **OFF** can be reached again only by setting Enable=0 from each state
- **Gray code** has been used to minimize transitions to a unwanted states




Note: We omitted the loops when ENABLE=1 or when the condition remains the same for the sake of clarity

MODALITY MANAGER

(Link to code: [ModalityManager.vhdl](#))

 - It is a **Moore FSM**
- The starting state is **MOD5**
- The modality can only be changed when the circuit is in the **MAINTENANCE** state
 - Otherwise the circuit ignores the modality change
- When Reset is set to 0 (Active Low) the FSM returns to MOD5




Note: We omitted the loops when RESET=1 or when the modality remains the same for the sake of clarity

LIGHT CONTROL SYSTEM

(Link to code: [LightControlSystem.vhdl](#))

- It is made by two sub-components:
 - **Control Logic:** a process that sets the lights according to the current condition and modality.
 - **Counter (w/ Reset):** a simple counter that keeps track of time
- By using both components, it is possible to handle the timings for the three lights
- The two components cooperate as follows:
 - The Control Logic can reset the Counter
 - The Counter is read by the Control Logic

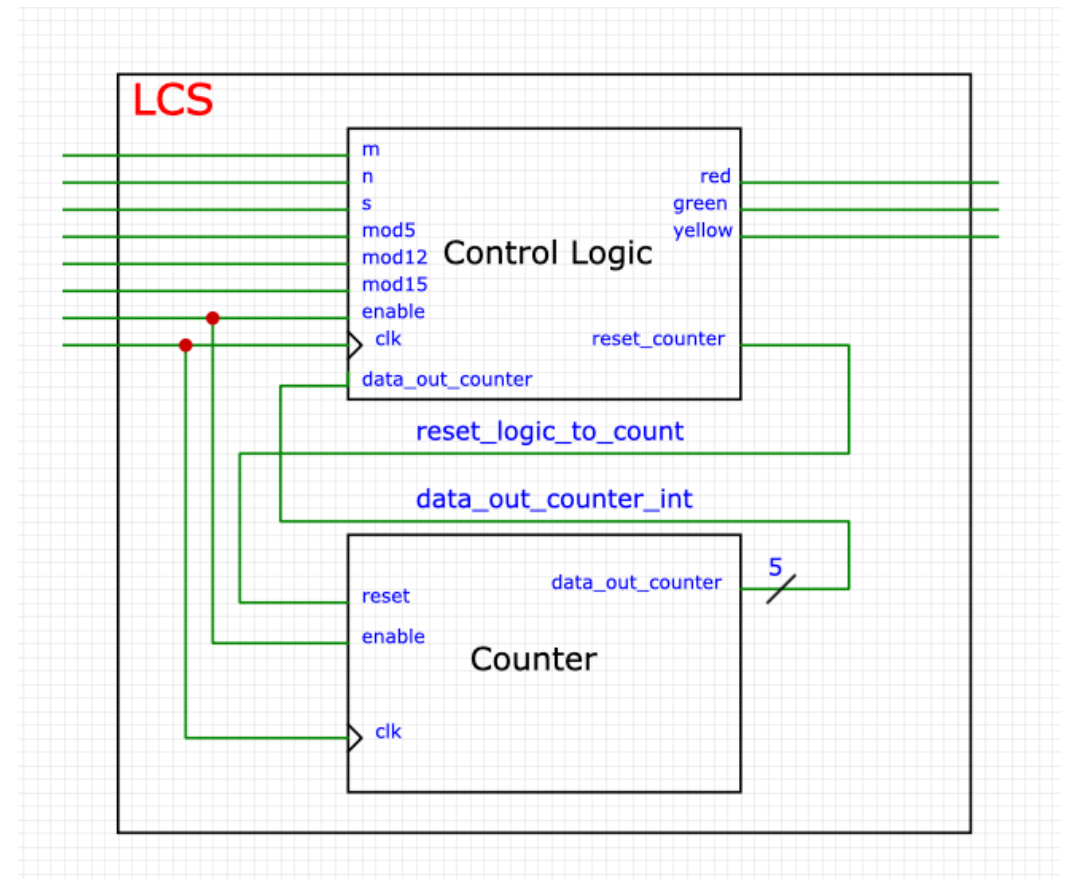


FAULT DETECTOR

(Link to code: [FaultDetector.vhdl](#))

- Detects whether or not the circuit is working correctly
- Takes as input the error bit from CM and MM
- Uses a **2x4 Decoder** for returning a bit sequence that represents the error type
- It is a **combinatory component**
- When an error is found, the **Enable** for the LCS is set to 0

Truth Table

enable	A1	A0	B3	B2	B1	B0
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

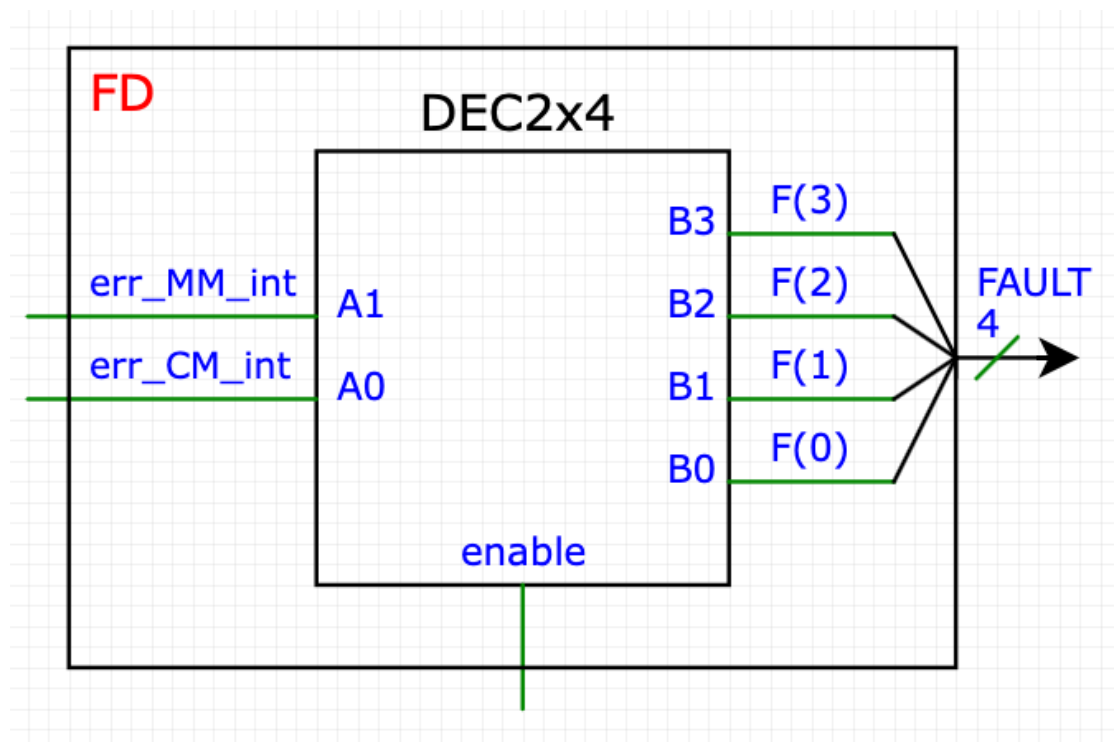




OUTLINE

- Introduction
- Symbol
 - I/O ports
- Top-view block scheme
 - Internal signals
 - VHDL Design of all stages
- **Simulation results**
- Conclusion


SIMULATION RESULTS

 Scenario #1: Everything working correctly




↑
OFF

SIMULATION RESULTS

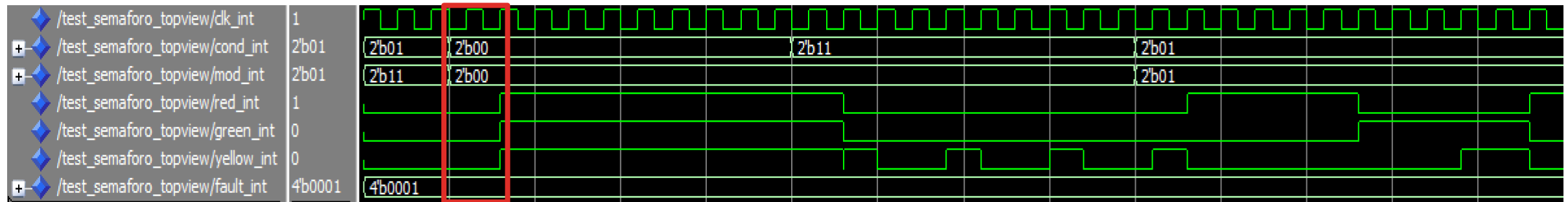


Delay between internal state change and lights update

SIMULATION RESULTS

 


MAINTENANCE

SIMULATION RESULTS

 


STANDBY

SIMULATION RESULTS

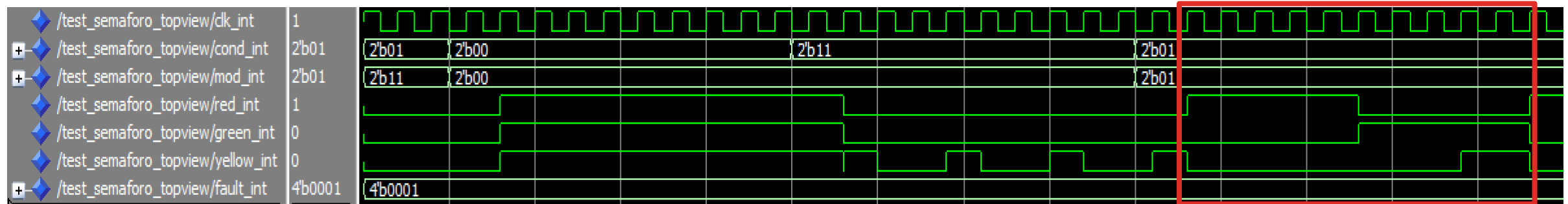


↑
NOMINAL
(MOD-5)

SIMULATION RESULTS

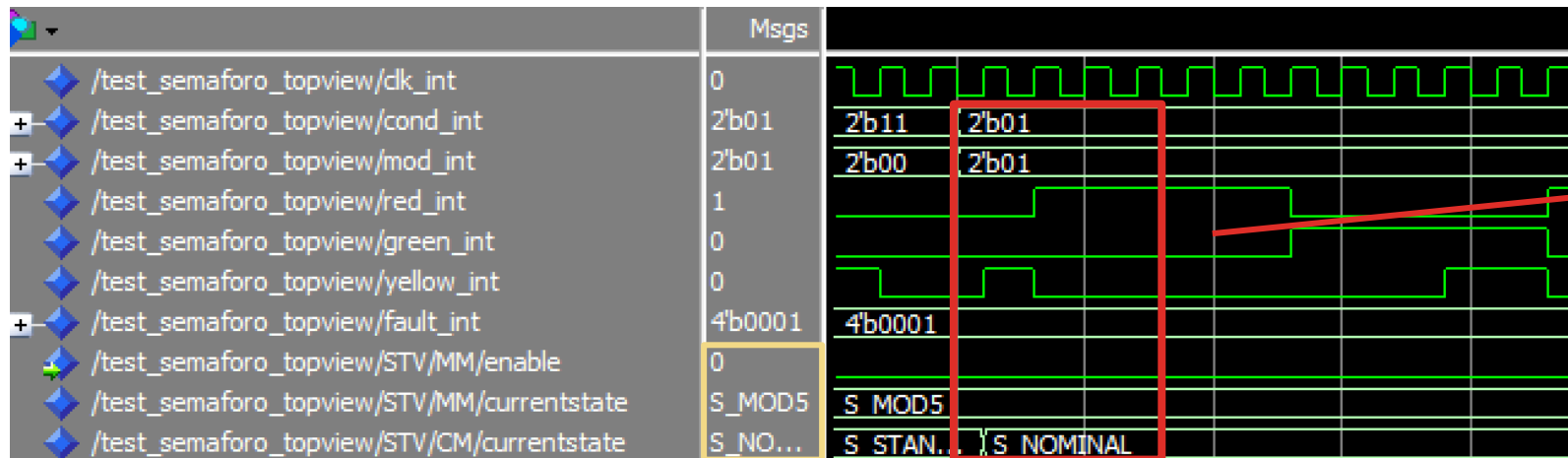


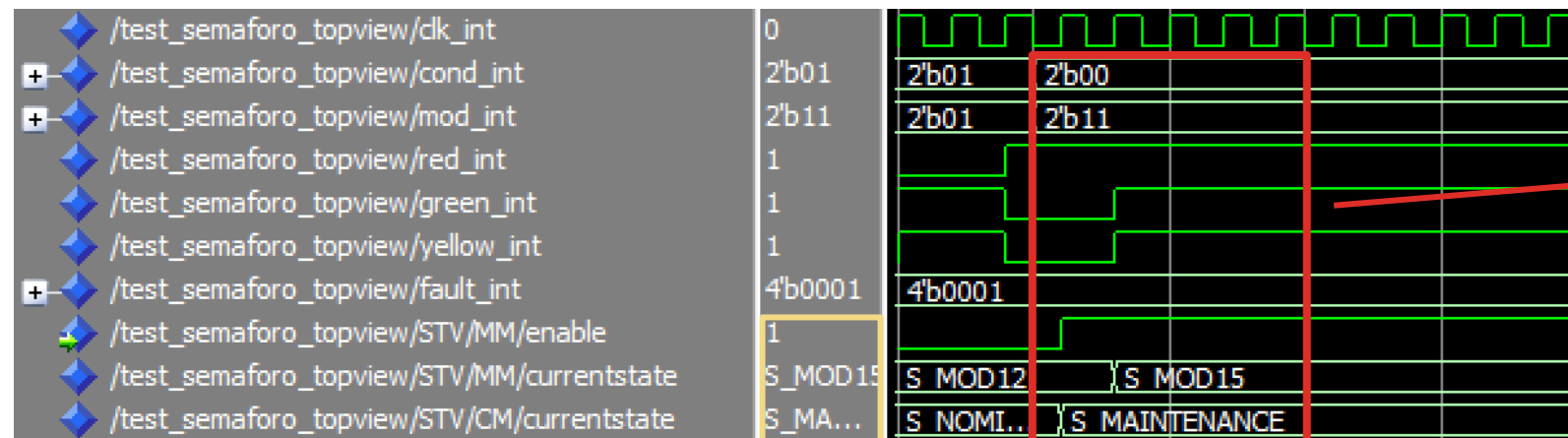The modality does not change since the traffic light is not in the MAINTENANCE state, therefore the Enable for Modality Manager is 0




The modality does change since the traffic light is in the MAINTENANCE state, therefore the Enable for Modality Manager is 1

SIMULATION RESULTS

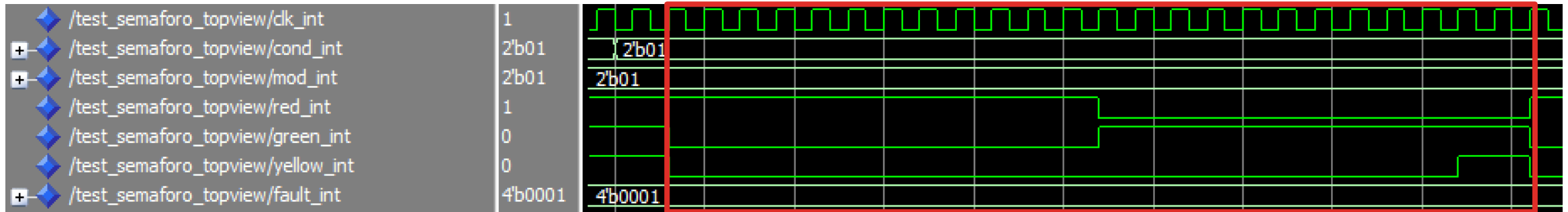

↑
NOMINAL
(MOD-12)


SIMULATION RESULTS

 

↑
NOMINAL
(MOD-15)


SIMULATION RESULTS

Scenario #2: FAULT Configuration

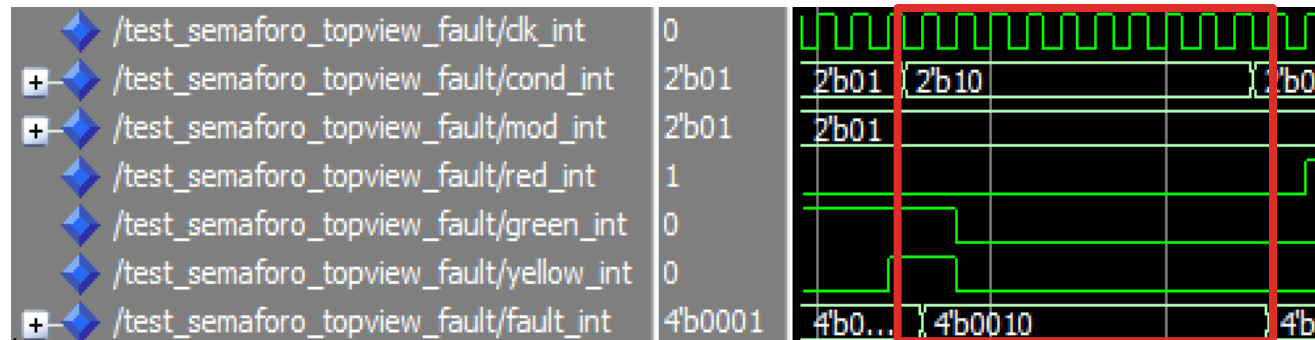


- 10 is an invalid input Condition, so Fault is set to 0010 that represents this type of error
- Lights are turned off until a valid Condition is set

SIMULATION RESULTS

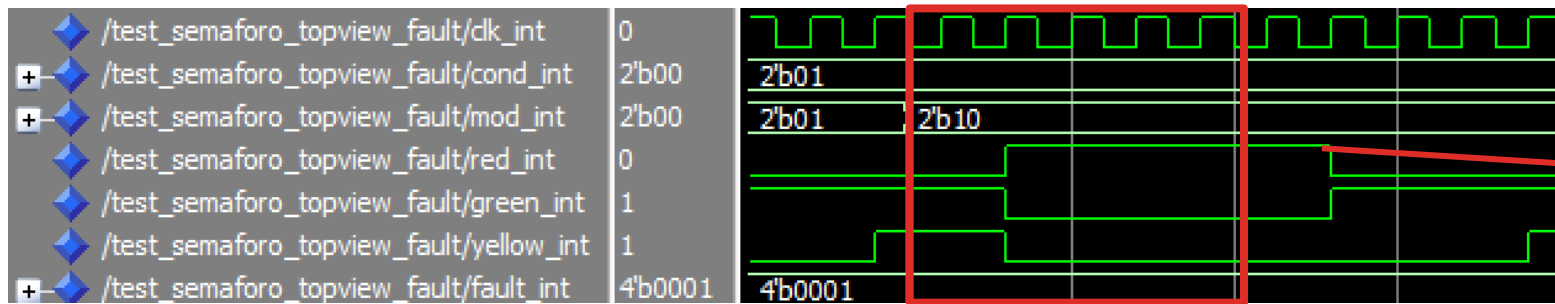


- 10 is an invalid input Modality, but it is ignored because the modality cannot be changed since the traffic light is not in the MAINTENANCE state

SIMULATION RESULTS

 

- 10 is an invalid input Modality, so Fault is set to 0100 that represents this type of error.
 - This is detected because the traffic light is in the MAINTENANCE state and therefore the Modality can be modified.
- Lights are turned off until a valid Condition is set


SIMULATION RESULTS

 

- 10 is an invalid input Condition
- 10 is an invalid input Modality
 - Fault is set to 1000 that represents an error on both
- Lights are turned off until a valid Condition is set

SIMULATION RESULTS

Scenario #3: Enable

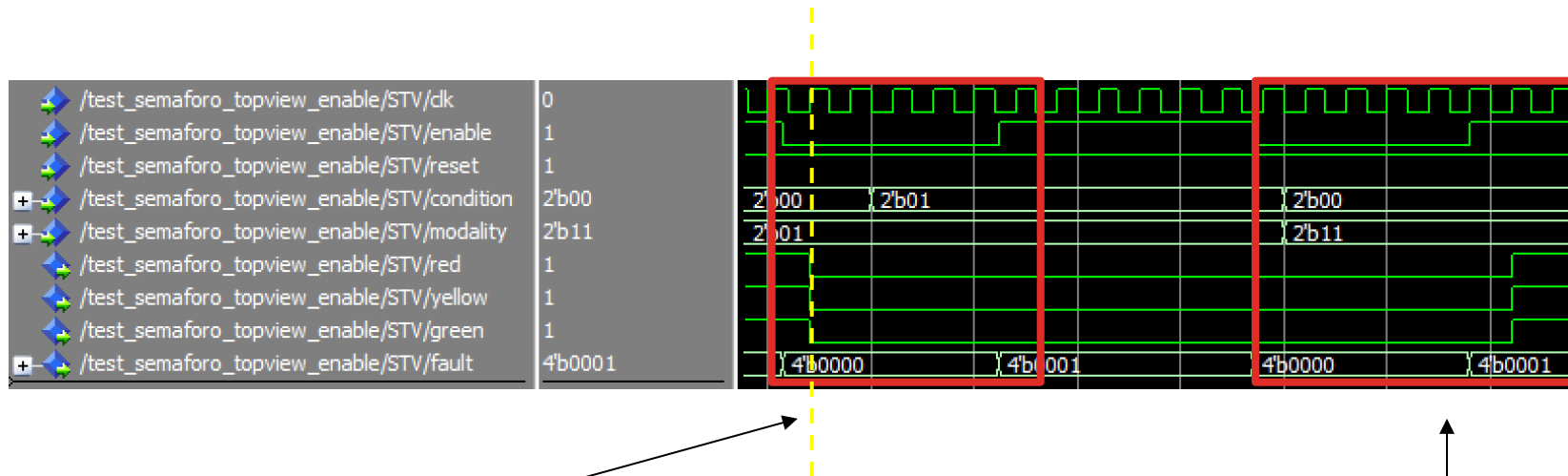

ENABLE:


- Active High
- Synchronous

All lights are off and it is not sensitive to condition changes

When ENABLE becomes 1 the OFF condition can be changed only by setting MAINTENANCE

SIMULATION RESULTS

Scenario #4: Reset

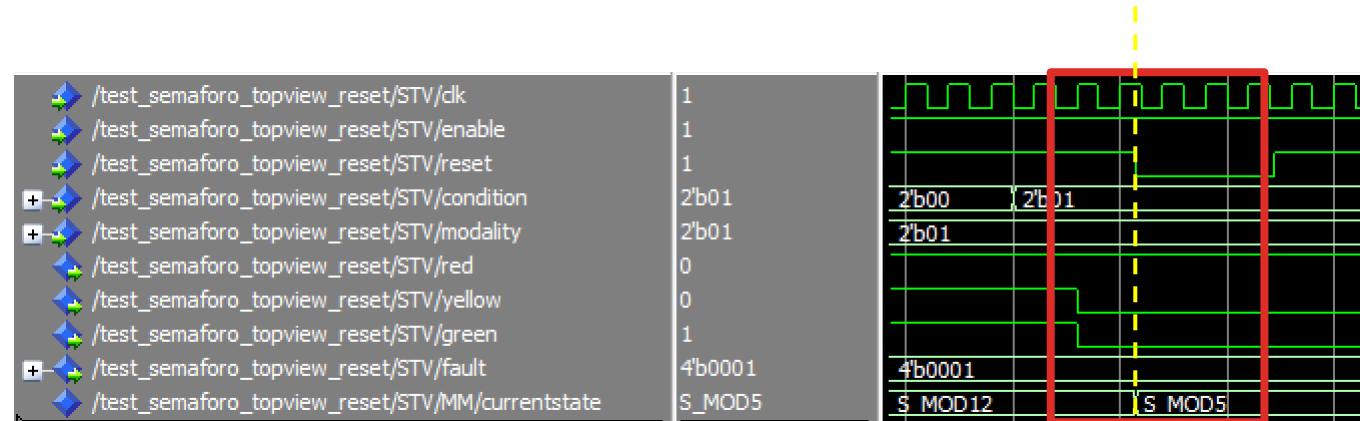


RESET:

- Active Low
- Asynchronous

When RESET becomes 0 the modality becomes MOD5

SIMULATION RESULTS

Scenario #5: Enable and Reset

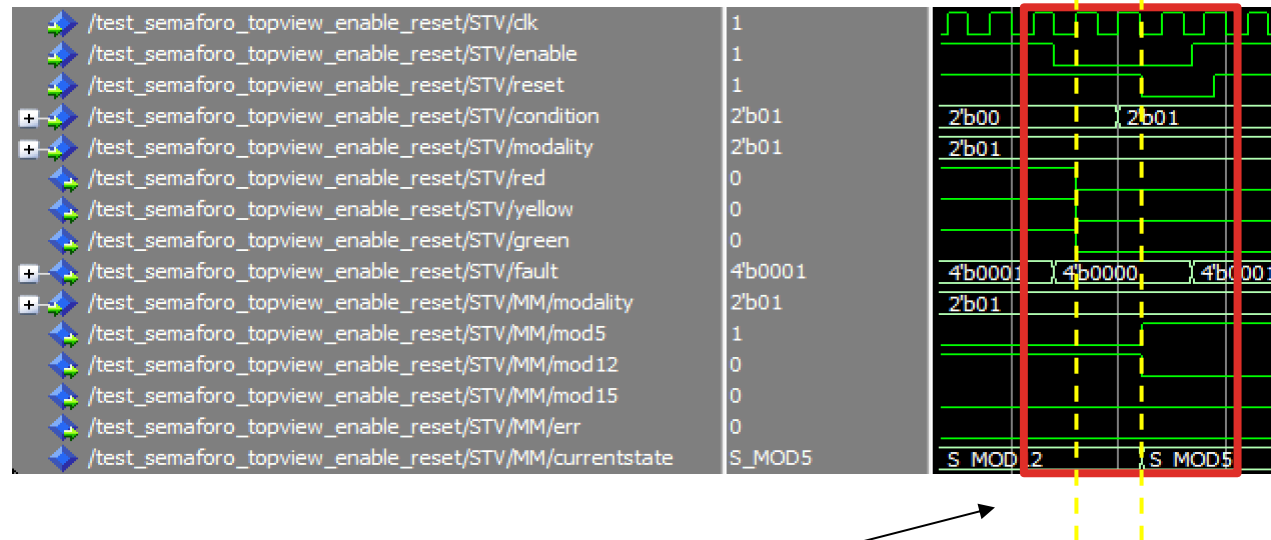

- RESET (Asynchronous) is priority over ENABLE (Synchronous)
- ENABLE = 0 makes the circuit insensitive to external signals and turns all the lights off
 - But when RESET = 0, the modality changes nonetheless



OUTLINE

- Introduction
- Symbol
 - I/O ports
- Top-view block scheme
 - Internal signals
 - VHDL Design of all stages
- Simulation results
- **Conclusion**



CONCLUSION

- Starting by the top-view block scheme, each component has been implemented in VHDL
- Each entity has been tested independently with its own testbench, before being connected
- As shown by the simulation results, and according to the initial assumptions, the circuit works as expected



OUTLINE

- Introduction
- Symbol
 - I/O ports
- Top-view block scheme
 - Internal signals
 - VHDL Design of all stages
- Simulation results
- Conclusion